

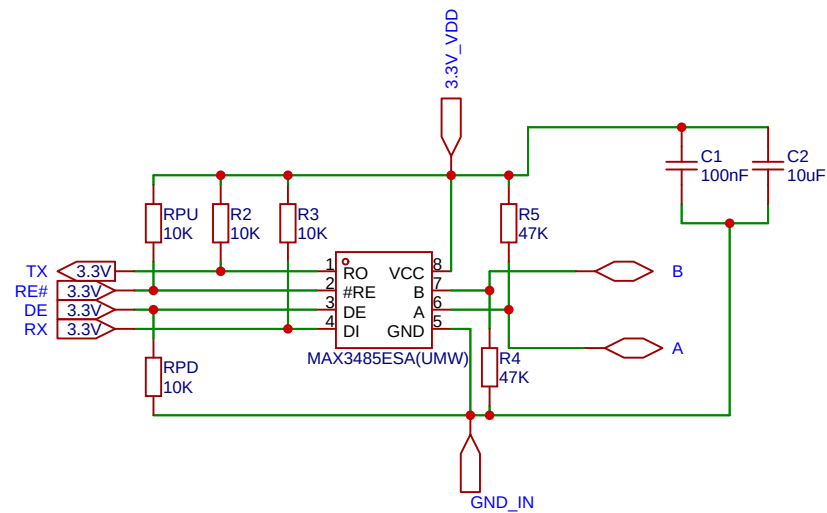


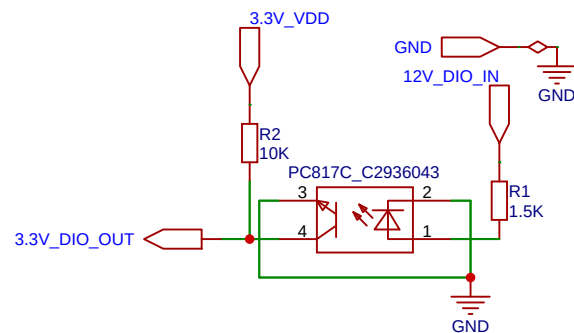


Schematic	RS485 to UART (3.3V)		Create at	2026-02-03
			Update at	2026-02-15
Board	RS485 to UART (3.3V)		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

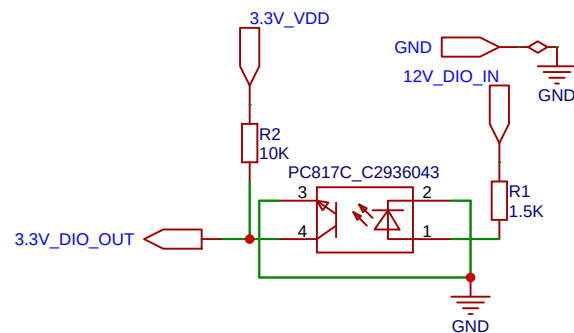


Schematic	12v dio to 3.3v dio		Create at	2026-02-04
			Update at	2026-02-15
Board	12v dio to 3.3v dio		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com




Schematic	12v dio to 3.3v dio_1		Create at	2026-02-04
			Update at	2026-02-15
Board	12v dio to 3.3v dio_1		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

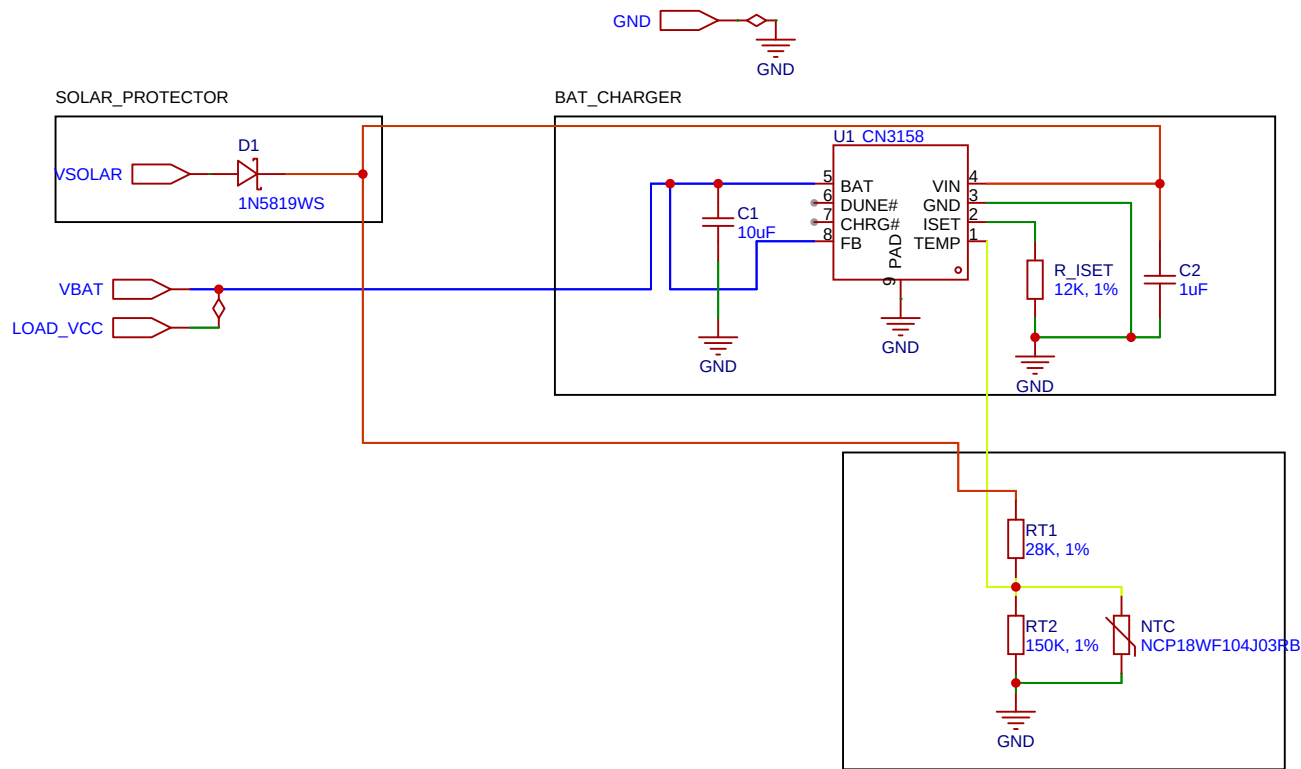


Schematic	SOLAR_CHARGER_1S			Create at	2026-02-03
				Update at	2026-02-15
Board	SOLAR_CHARGER_1S			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
	Version	Size	Page 1 Total 1		
EasyEDA		V1.0	A4	EasyEDA.com	

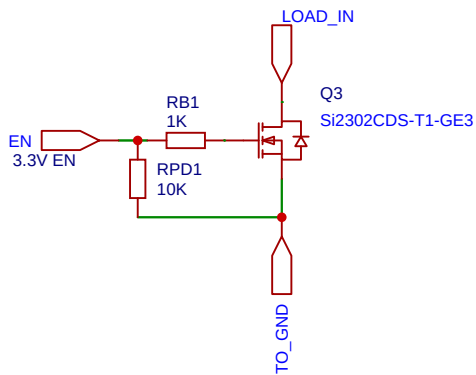


Schematic	12V-0.1A N-CHANNEL_1			Create at	2026-02-04
				Update at	2026-02-15
Board	12V-0.1A N-CHANNEL_1			Page	P1
Drawn		REVITA_LINK_v1			
Reviewed					
		Version	Size	Page 1 Total 1	
		V1.0	A4	EasyEDA.com	

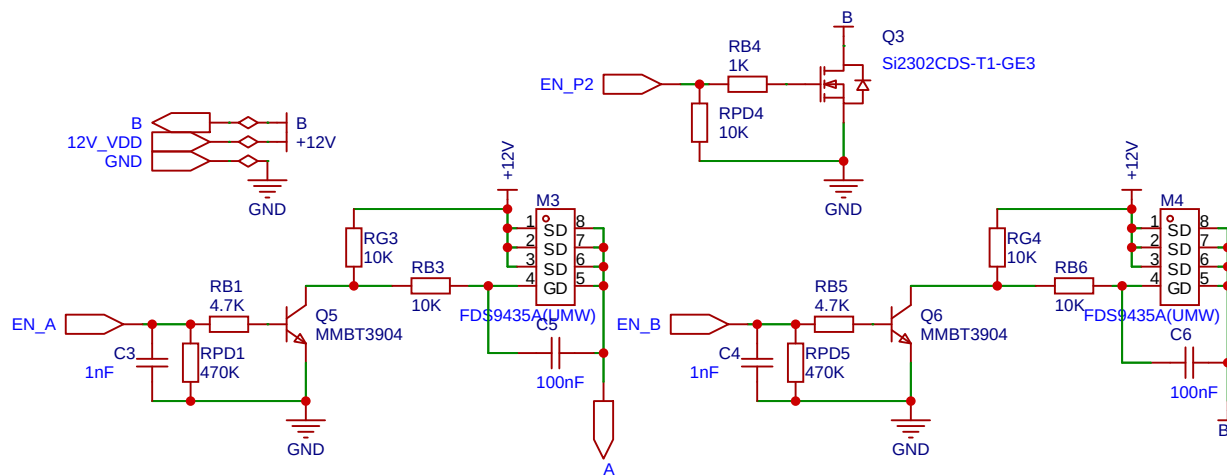


Schematic	3-Line-motor-control			Create at	2026-02-03
				Update at	2026-02-15
Board	3-Line-motor-control			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
	Version	Size	Page 1 Total 1		
EasyEDA		V1.0	A4	EasyEDA.com	

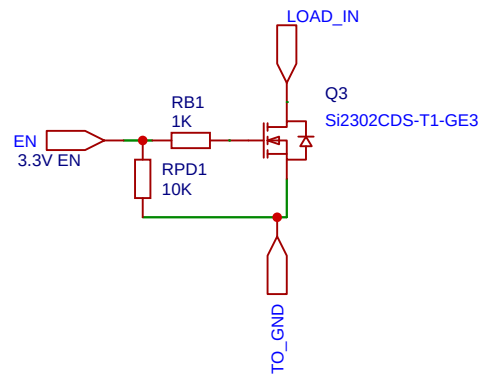


Schematic	12V-0.1A N-CHANNEL		Create at	2026-02-04
			Update at	2026-02-15
Board	12V-0.1A N-CHANNEL		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

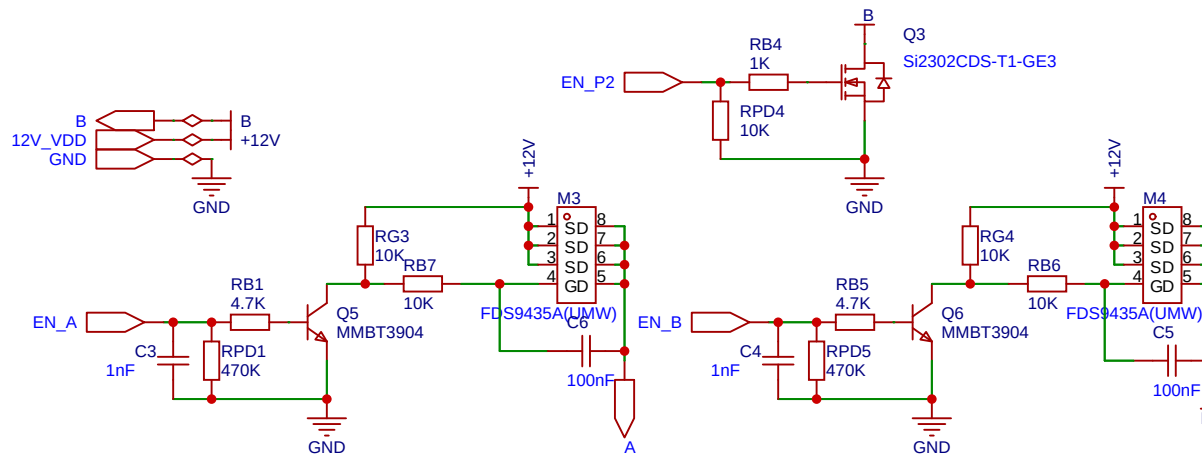

Schematic	3-Line-motor-control_1			Create at	2026-02-04
				Update at	2026-02-15
Board	3-Line-motor-control_1			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
		Version	Size	Page 1 Total 1	
		V1.0	A4	EasyEDA.com	

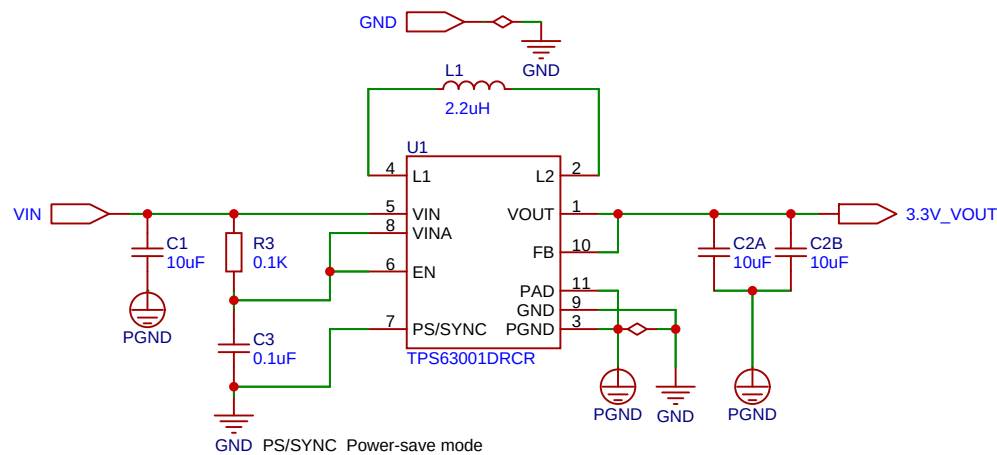


Schematic	3.3V_buck_boost		Create at	2026-02-03
			Update at	2026-03-11
Board	3.3V_buck_boost		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

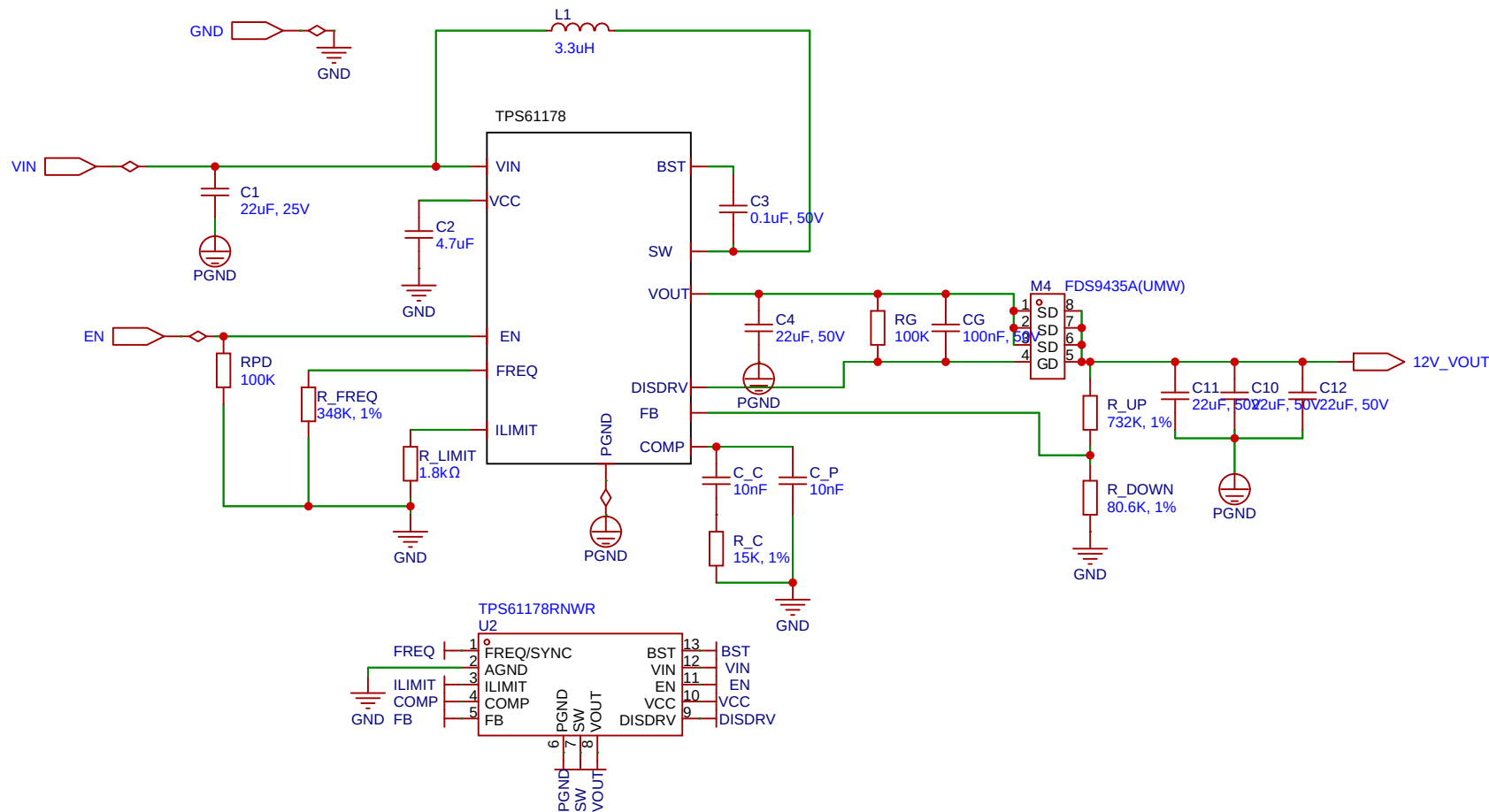


Schematic	12V-step-up_1			Create at	2026-02-13
				Update at	2026-03-18
Board	12V-step-up			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
	Version		Size	Page 1 Total 1	
EasyEDA		V1.0	A4	EasyEDA.com	


POWER_PORT

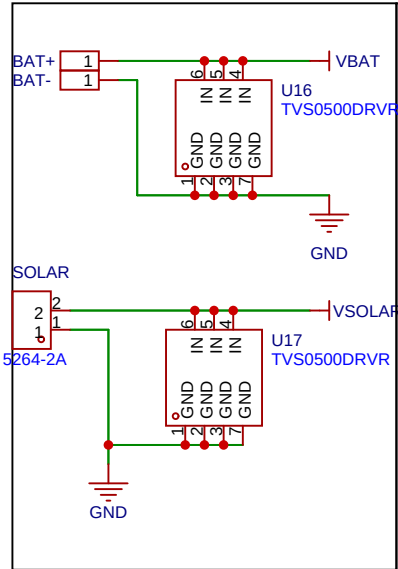


POWER_IC

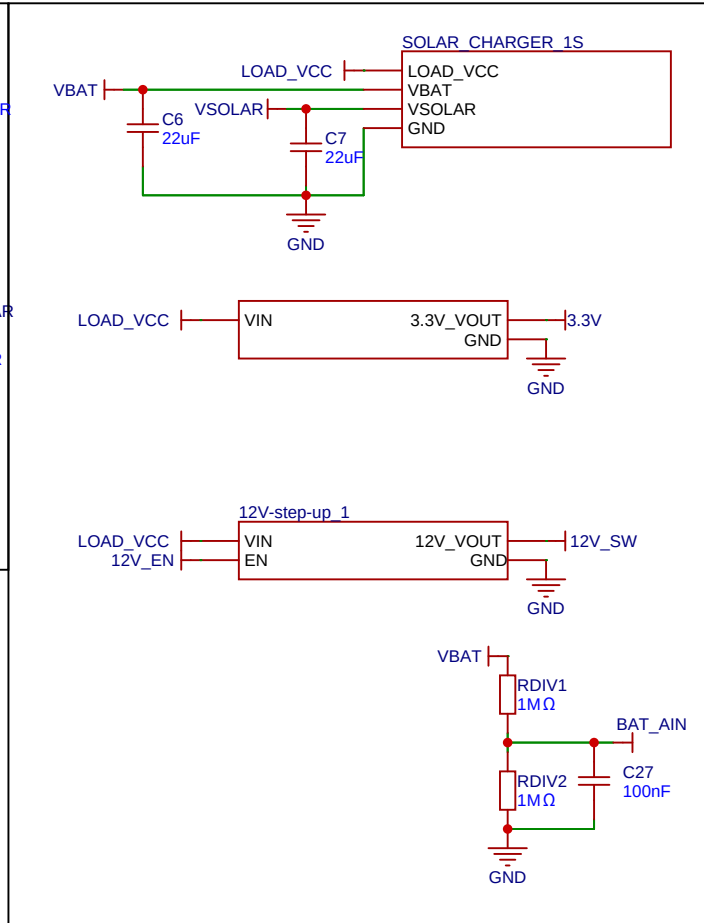


MCU_PART

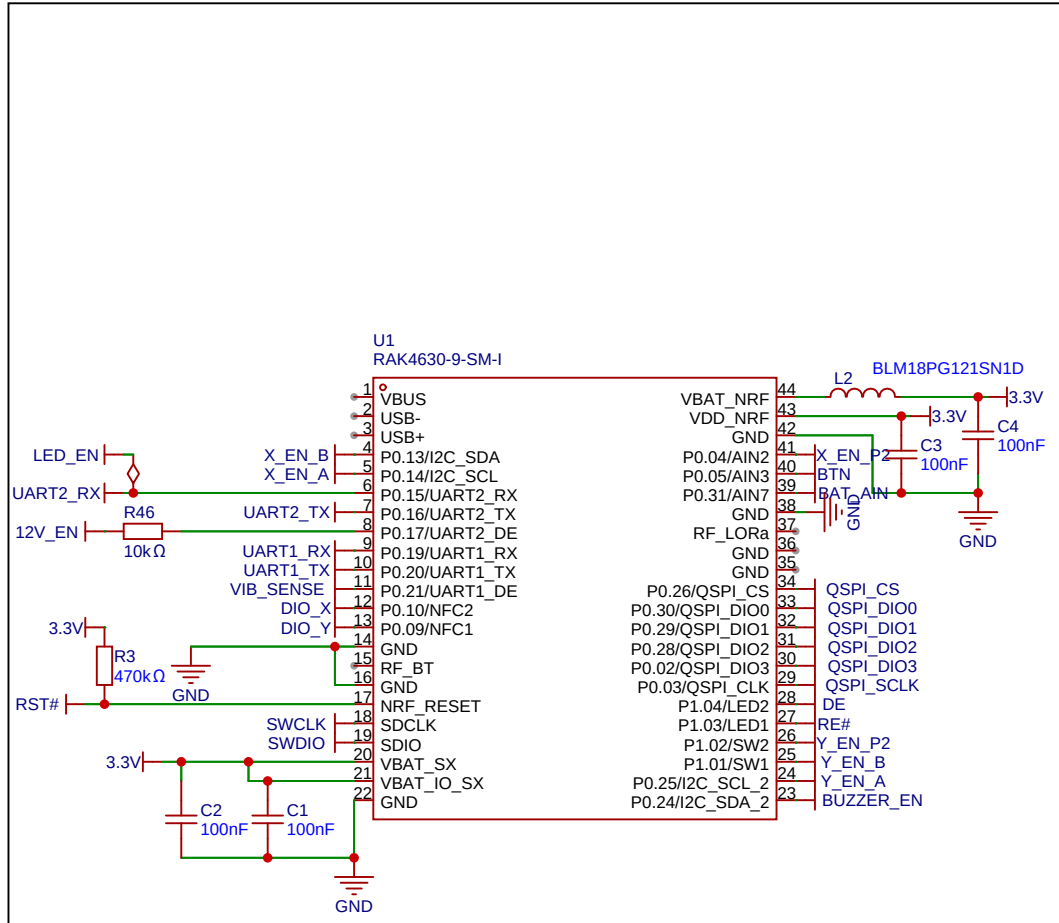


STLINK_PORT

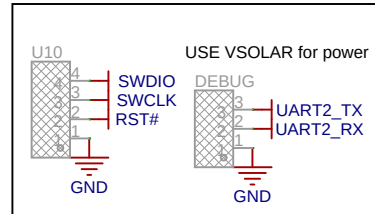


EXTERNAL_BUTTON

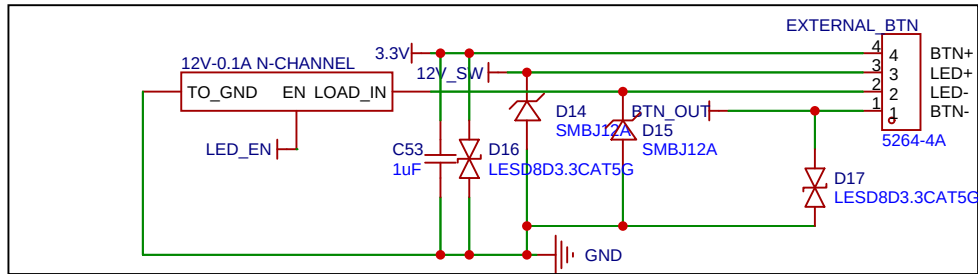



BUTTON DECOUPLER

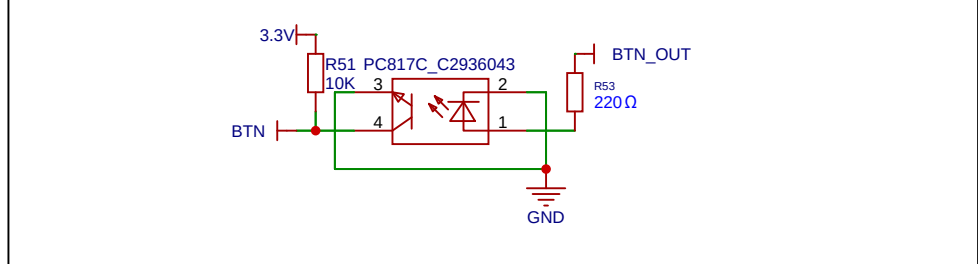


FLASH_MEMORY

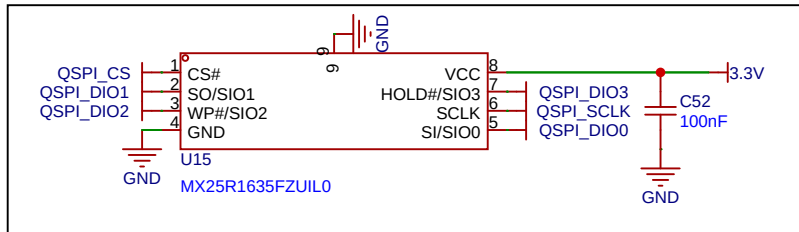


ANTI_THEIF

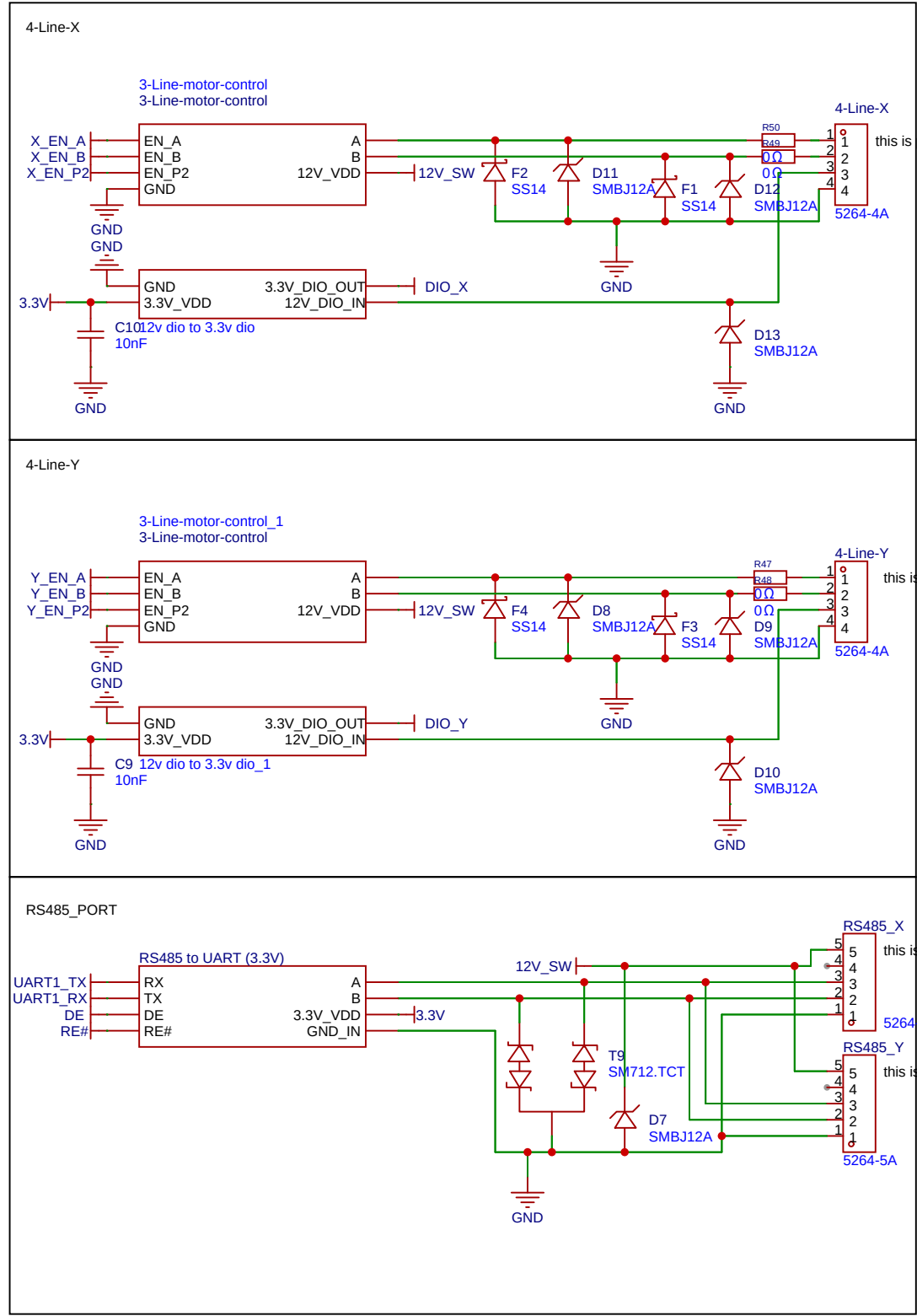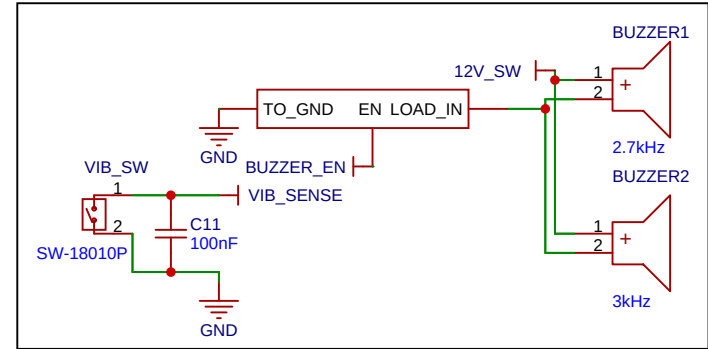


Schematic	Schematic1			Create at	2026-02-01
Board	main_board			Update at	2026-04-09
Drawn		REVITA_LINK_v1			
Reviewed					
		Version	Size	Page 1 Total 1	
EasyEDA		V1.0	A4	EasyEDA.com	

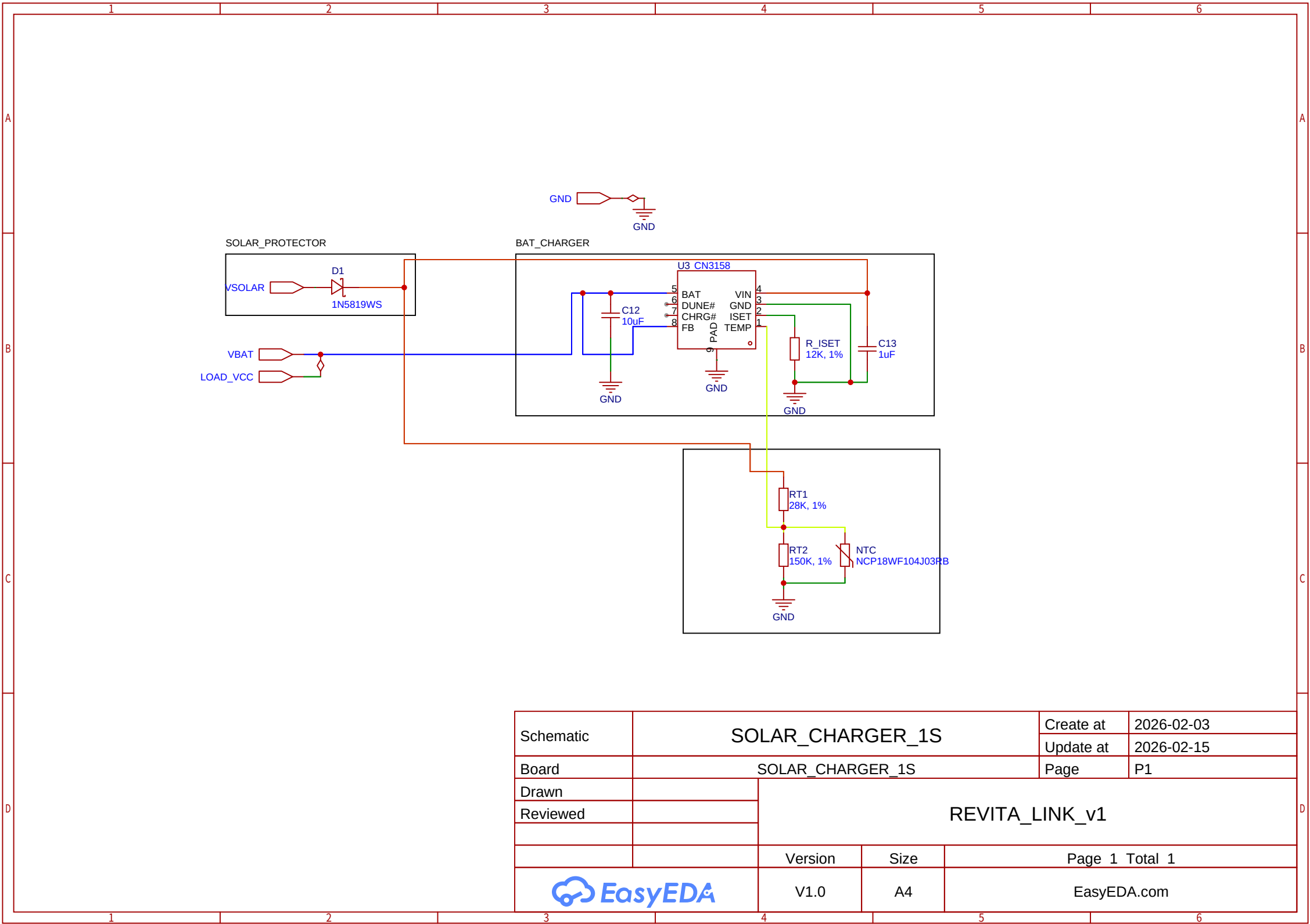


Schematic	SOLAR_CHARGER_1S	Create at	2026-02-03
		Update at	2026-02-15
Board	SOLAR_CHARGER_1S	Page	P1
Drawn	REVITA_LINK_v1		
Reviewed			
	Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4
		EasyEDA.com	

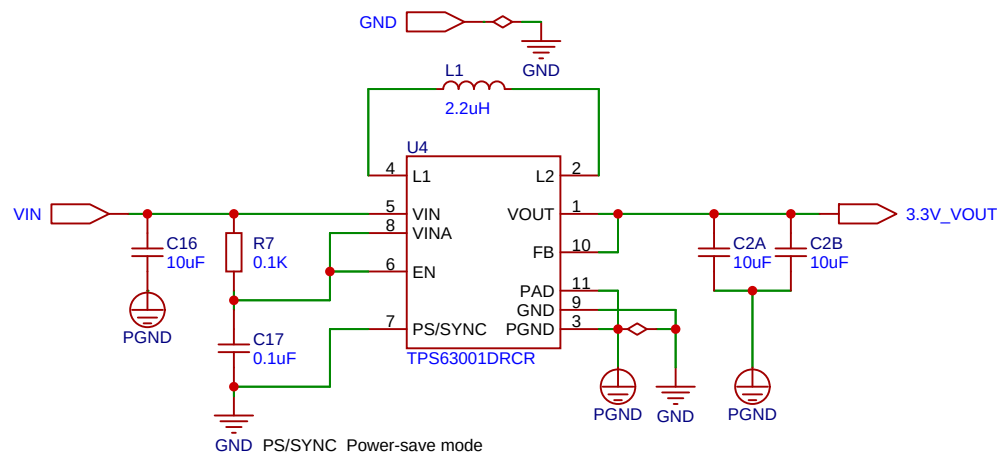


Schematic	3.3V_buck_boost			Create at	2026-02-03
				Update at	2026-03-11
Board	3.3V_buck_boost			Page	P1
Drawn		REVITA_LINK_v1			
Reviewed					
		Version	Size	Page 1 Total 1	
		V1.0	A4	EasyEDA.com	

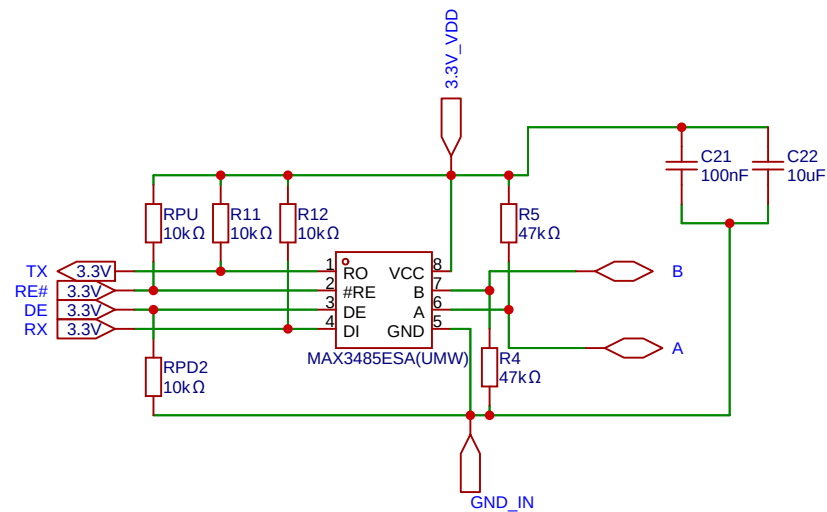


Schematic	RS485 to UART (3.3V)		Create at	2026-02-03
			Update at	2026-02-15
Board	RS485 to UART (3.3V)		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

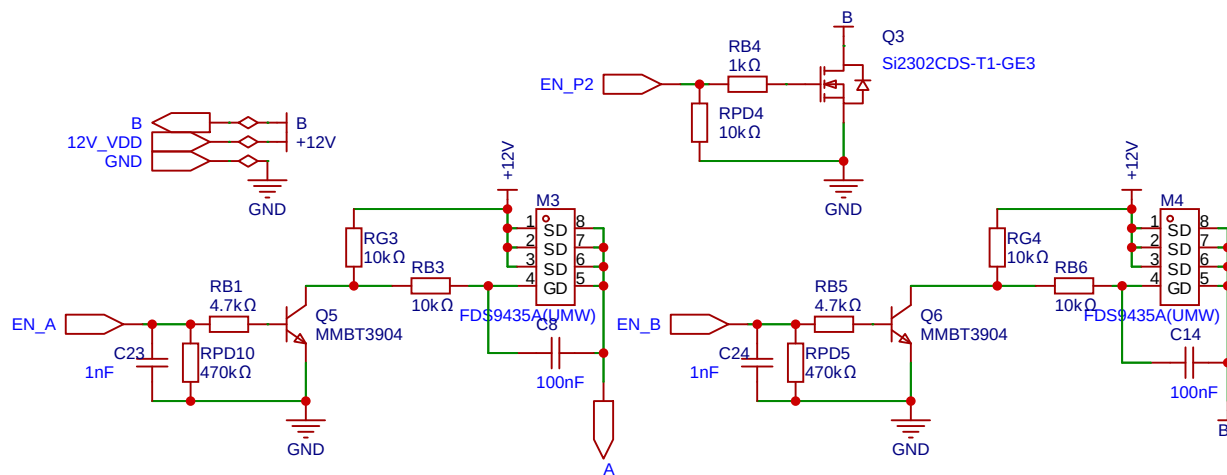


Schematic	3-Line-motor-control			Create at	2026-02-03
				Update at	2026-02-15
Board	3-Line-motor-control			Page	P1
Drawn		REVITA_LINK_v1			
Reviewed					
		Version	Size	Page 1 Total 1	
EasyEDA		V1.0	A4	EasyEDA.com	

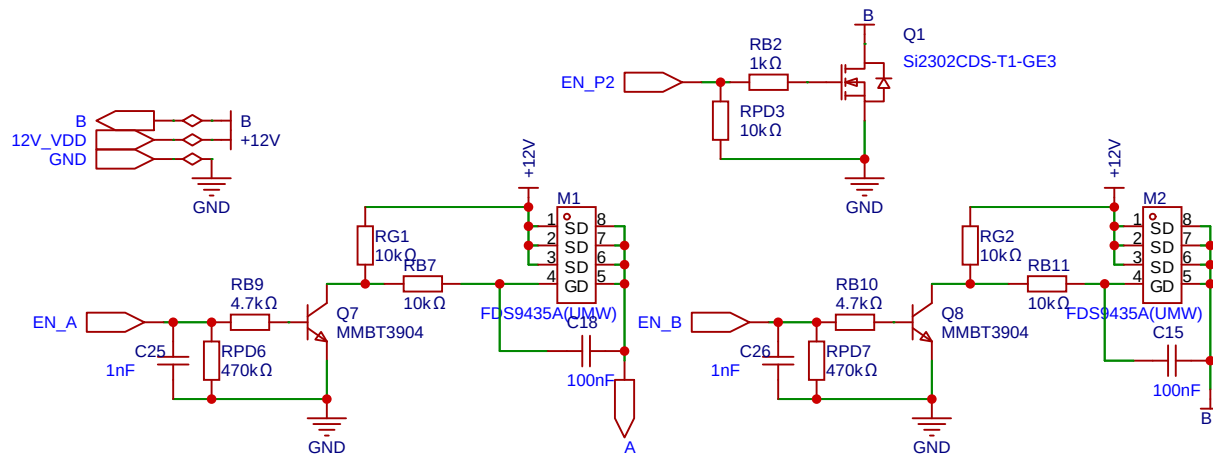


Schematic	3-Line-motor-control_1			Create at	2026-02-04
				Update at	2026-02-15
Board	3-Line-motor-control_1			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
		Version	Size	Page 1 Total 1	
		V1.0	A4	EasyEDA.com	

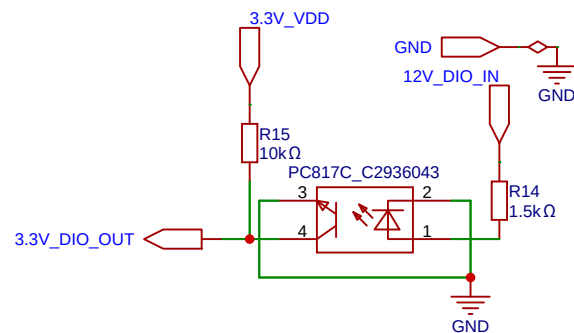


Schematic	12v dio to 3.3v dio			Create at	2026-02-04
				Update at	2026-02-15
Board	12v dio to 3.3v dio			Page	P1
Drawn		REVITA_LINK_v1			
Reviewed					
		Version	Size	Page 1 Total 1	
EasyEDA		V1.0	A4	EasyEDA.com	

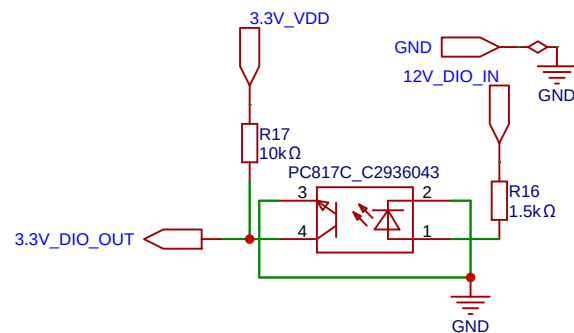


Schematic	12v dio to 3.3v dio_1		Create at	2026-02-04
			Update at	2026-02-15
Board	12v dio to 3.3v dio_1		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

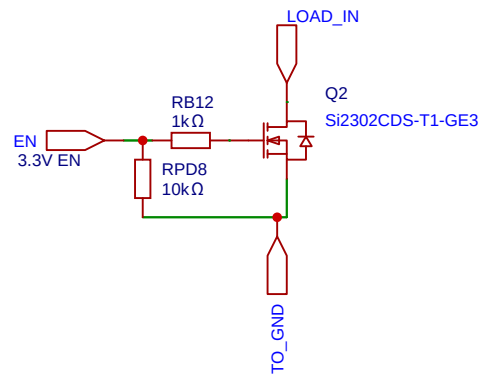

Schematic	12V-0.1A N-CHANNEL		Create at	2026-02-04
			Update at	2026-02-15
Board	12V-0.1A N-CHANNEL		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

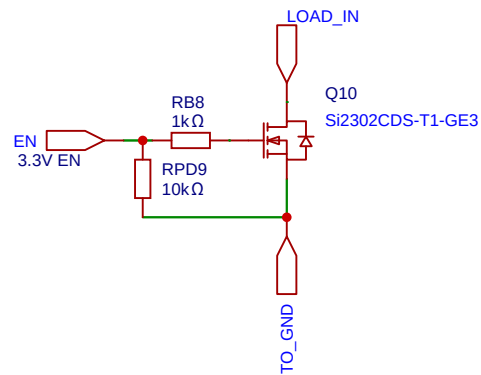

Schematic	12V-0.1A N-CHANNEL_1		Create at	2026-02-04
			Update at	2026-02-15
Board	12V-0.1A N-CHANNEL_1		Page	P1
Drawn		REVITA_LINK_v1		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com

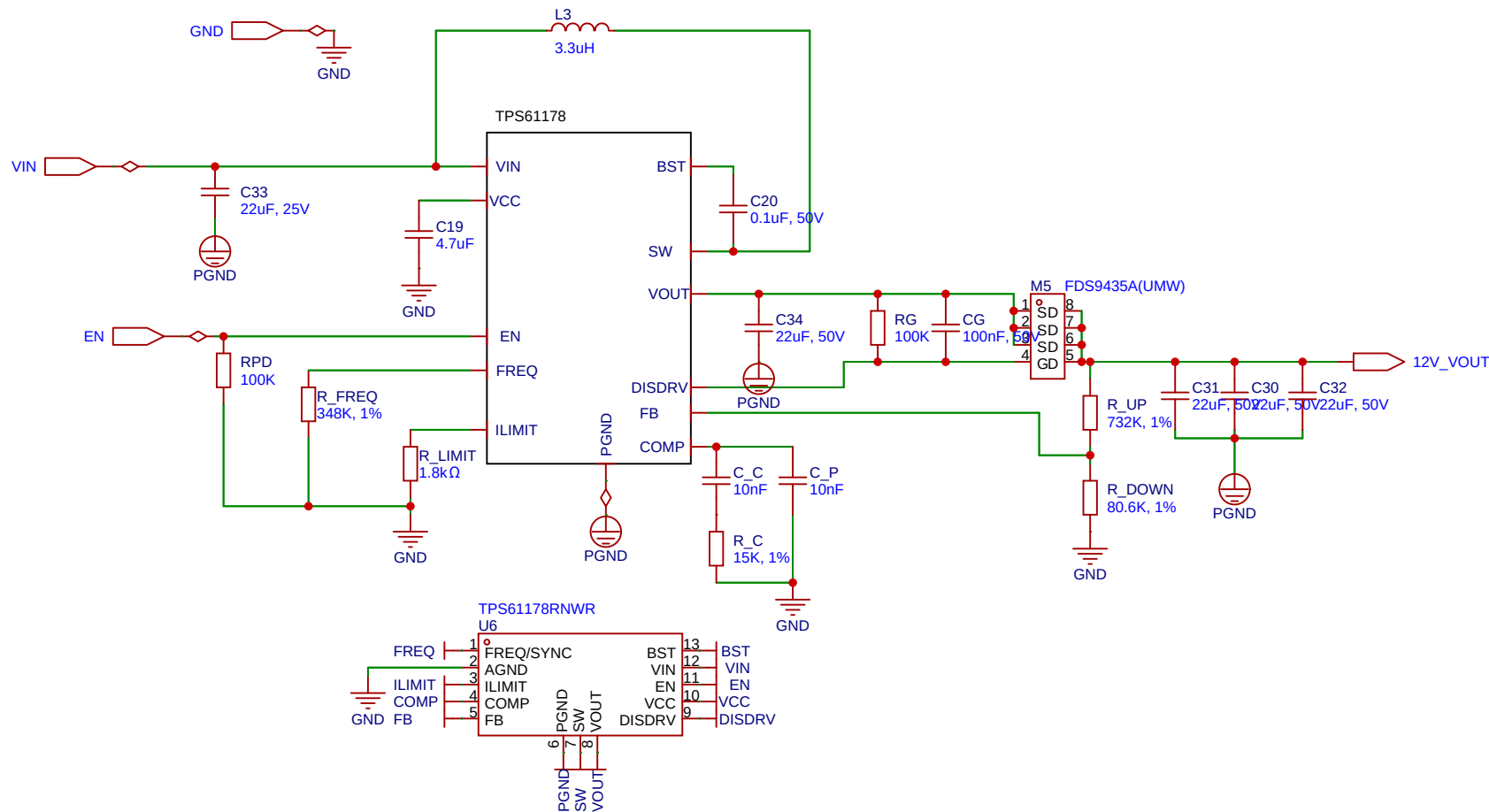

Schematic	12V-step-up_1			Create at	2026-02-13
				Update at	2026-03-18
Board	12V-step-up			Page	P1
Drawn	REVITA_LINK_v1				
Reviewed					
		Version	Size	Page 1 Total 1	
EasyEDA		V1.0	A4	EasyEDA.com	